


**03 – LOW NOISE AMPLIFIERS FOR FM RECEIVERS**

18/10/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)


04/06/2020 (rev.1 exam 12/06/2020)

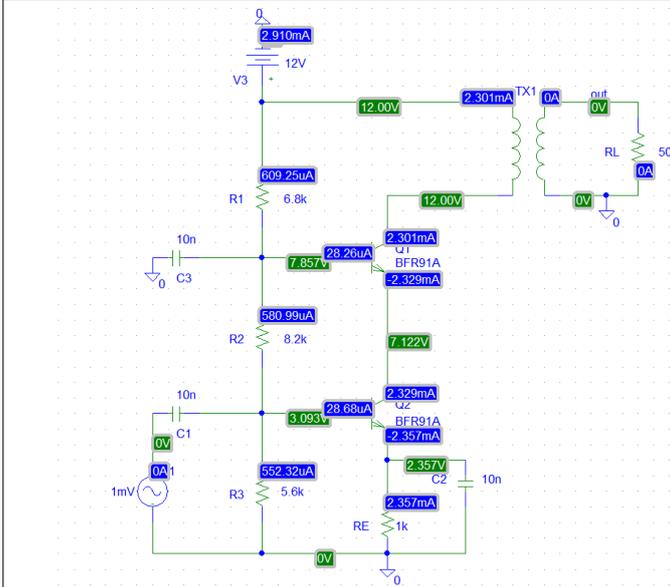**POINT 1**

Draw the cascode circuit and insert the output transformer placing an “XFRM\_LINEAR” component. Set the value of inductances  $L1$  and  $L2$  in order to have an unitary transformation ratio with an inductance of 100nH. Check the bias operation point and, by means of an AC analysis, determine the midband voltage gain of the amplifier. Comment on the results.





Transistors are polarized in right way

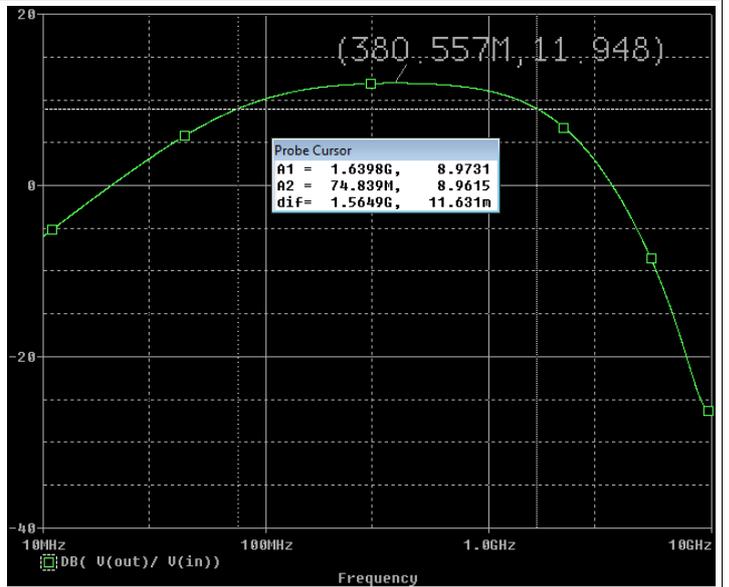

Maximum gain 12dB at 380,56 MHz  
Bandwidth 1,56 GHz

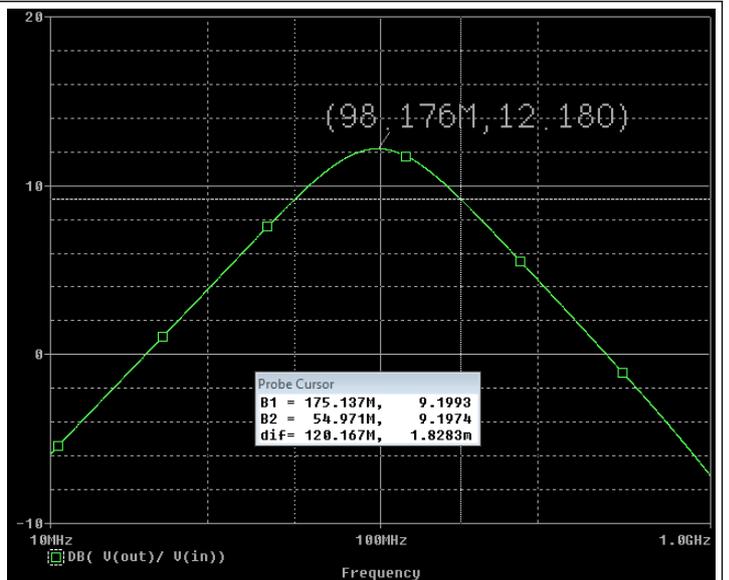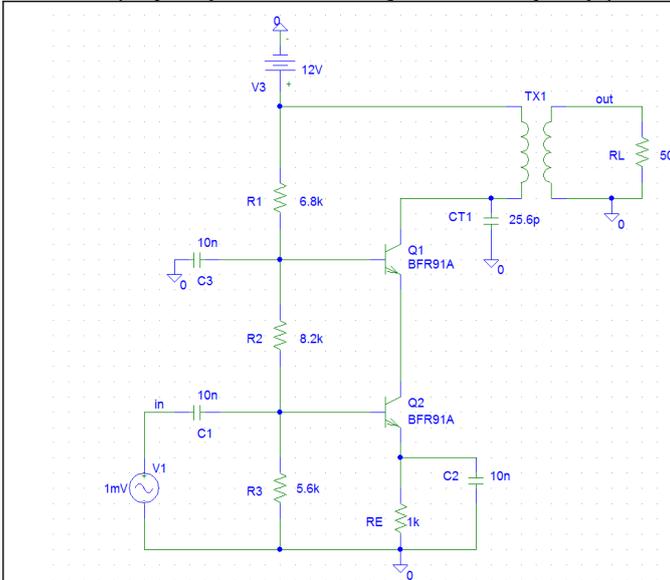**POINT 2**

Insert the tuning capacitor  $CT1$  imposing a center frequency of 98MHz. Plot the frequency response of the amplifier and measure the resonance frequency, the maximum gain and the quality factor  $Q$  of the circuit.



$CT1 = 25,6 \text{ pF}$   
Maximum gain 12,2 dB at 98,176 MHz  
Bandwidth = 120,167 MHz

$$Q = \frac{f_0}{BW} \approx 0,82$$

**03 – LOW NOISE AMPLIFIERS FOR FM RECEIVERS**

18/10/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)

04/06/2020 (rev.1 exam 12/06/2020)

**POINT 3**

As shown in Fig.3, add a type L matching network on the output of the transformer in order to obtain a voltage gain greater than 35dB at the resonance. For the design of L network use the online tools presented in the previous exercise: <http://home.sandiego.edu/~ekim/e194rfs01/jwmatcher/matcher2.html>

$$(A_v)_{dB} = 35 \text{ dB} \rightarrow A_v = 56,23$$

\*\*\*\* BIPOLAR JUNCTION TRANSISTORS

NAME	Q_Q1	Q_Q2
MODEL	BFR91A	BFR91A
IB	2.83E-05	2.87E-05
IC	2.30E-03	2.33E-03
VBE	7.35E-01	7.36E-01
VBC	-4.14E+00	-4.03E+00
VCE	4.88E+00	4.76E+00
BETADC	8.14E+01	8.12E+01
GM	8.80E-02	8.91E-02
RPI	9.37E+02	9.23E+02
RX	1.00E+01	1.00E+01
RO	1.93E+04	1.90E+04
CBE	4.10E-12	4.11E-12
CBC	6.09E-13	6.12E-13
CJS	0.00E+00	0.00E+00
BETAAC	8.25E+01	8.23E+01
CBX/CBX2	0.00E+00	0.00E+00
FT/FT2	2.97E+09	3.00E+09

Using an approximated formula

$$A_v = -\frac{R_{in}}{R_s + R_{in}} g_{m2} R_L$$

and

$$R_{in} = R_{B1} // R_{B2} // r_{\pi 1}$$

$$R_s = -\left( \frac{R_{in}}{A_v} g_{m2} R_L + R_{in} \right)$$

$$R_{in} = 731 \Omega$$

Using Impedance Matching Network Designer

Input values


Source Resistance:  Source Reactance:

Load Resistance:  Load Reactance:

Desired Q:  Frequency:

Output values



LOWPASS Hi-Low MATCHING NETWORK

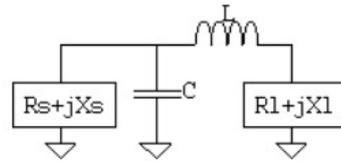

L Value:  nH

C Value:  pF

Q Value:

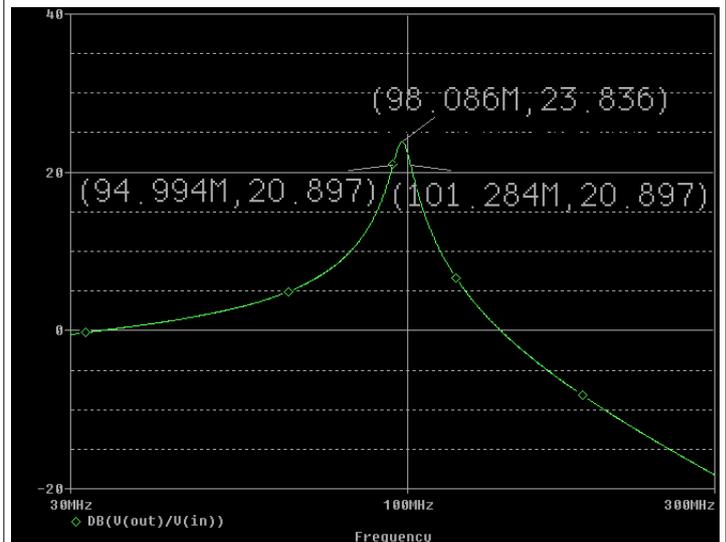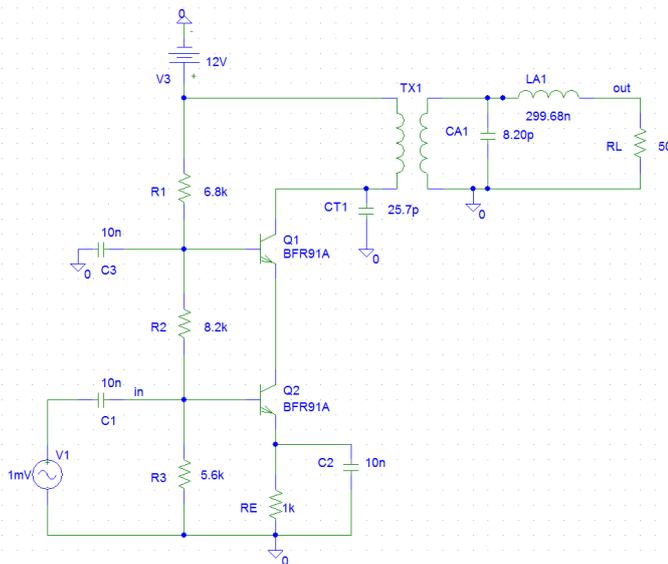

Maximum gain 23,84 dB at 98,086 MHz, Bandwidth 6,2 MHz, Q=15,82

You can note that the maximum gain is 24 dB. This behavior arise from approximations in expression of gain.

**03 – LOW NOISE AMPLIFIERS FOR FM RECEIVERS**

18/10/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)



04/06/2020 (rev.1 exam 12/06/2020)

The influence of the output resistance should be inserted increasing the value of Rin (called Rs in the online tool).

Executing several simulation you can obtain the following results

Rs (Ohm)	Gain (dB)	BW (MHz)
731	23.80	6.20
1000	25.20	4.60
<b>2000</b>	<b>28.10</b>	<b>2.55</b>
5000	32.00	...
10000	35.10	0.56

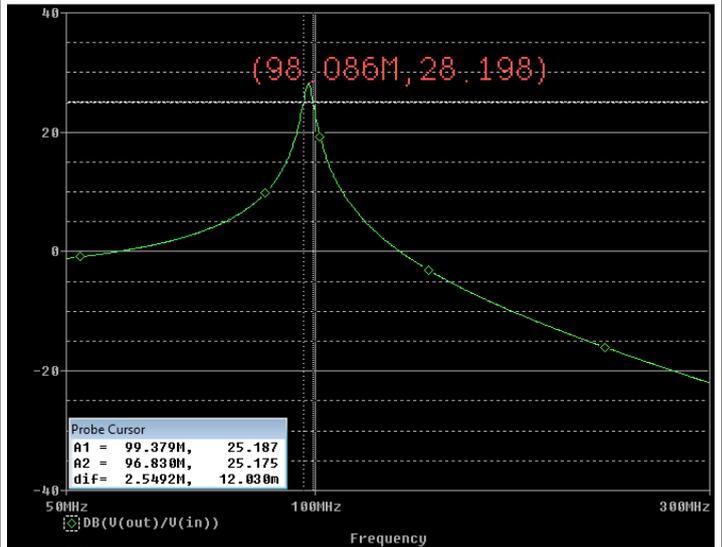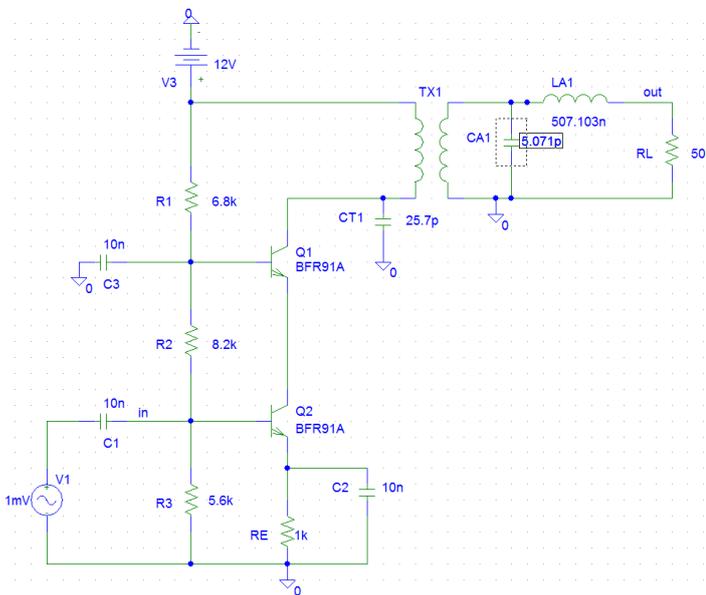Using configuration with 35dB of gain the bandwidth is too selective, for this reason the configuration with 28 dB is used in the following development.



Maximum gain 28,2 dB at 98,086 MHz, Bandwidth 2.55 MHz, Q=38,46


**03 – LOW NOISE AMPLIFIERS FOR FM RECEIVERS**

18/10/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)


04/06/2020 (rev.1 exam 12/06/2020)

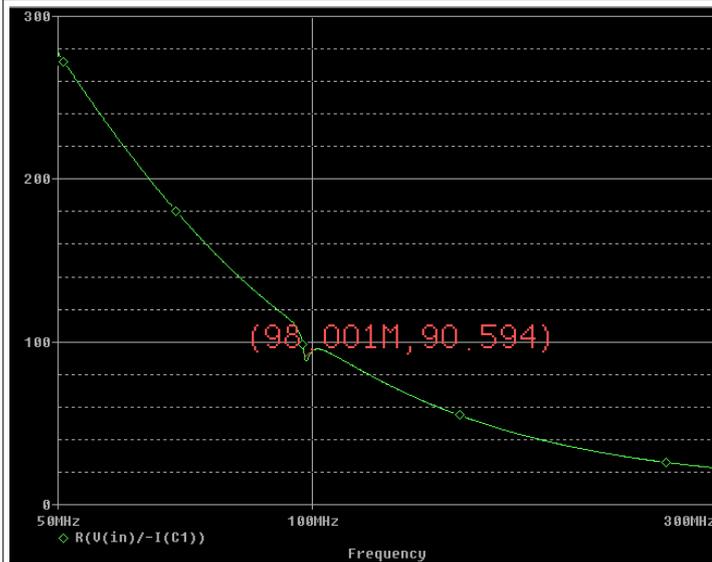**POINT 4**

After the design of the output matching network, determine the real and imaginary part of the input impedance of the circuit at the center frequency (98MHz).



Real part of input impedance = 90,59

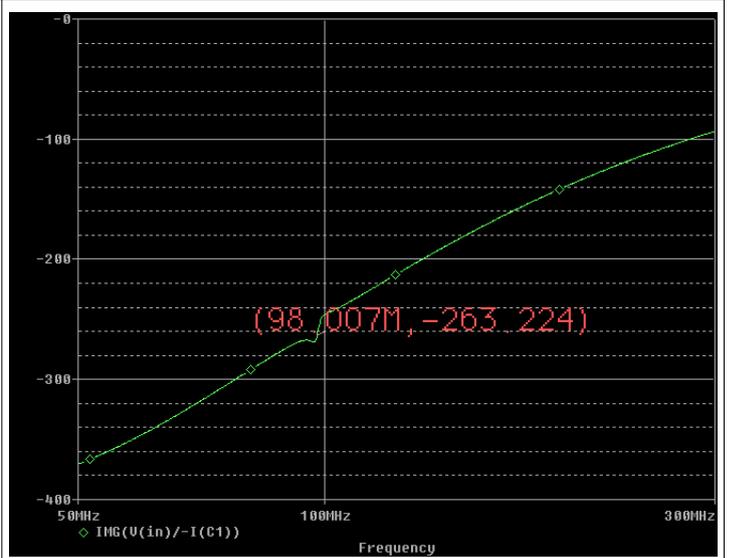

Imaginary part of input impedance = -263,22


Calculate the values of the input matching network (L type) in order to have the maximum power transfer.

Source Resistance:  Source Reactance:

Load Resistance:  Load Reactance:

Desired Q:  Frequency:

**LOWPASS Low-Hi MATCHING NETWORK**

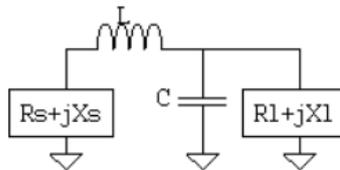

L Value:  nH

C Value:  pF


Q Value:

**03 – LOW NOISE AMPLIFIERS FOR FM RECEIVERS**

18/10/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)


04/06/2020 (rev.1 exam 12/06/2020)

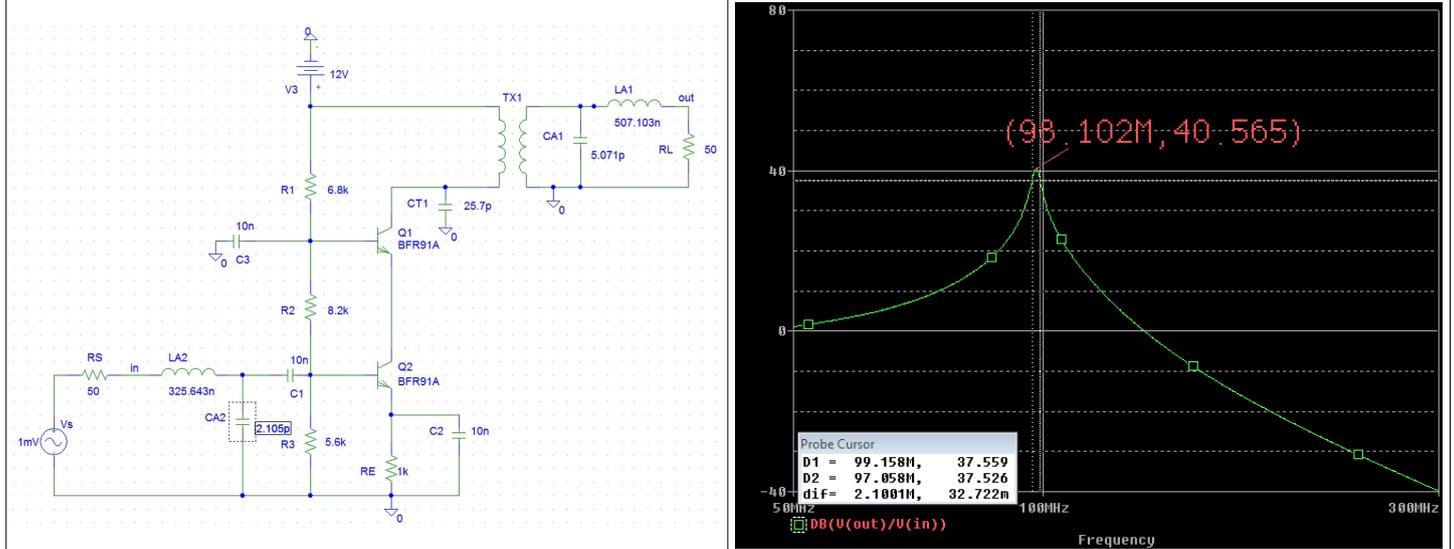Insert the matching network in the circuit as in Fig. 4. Plot the frequency response of the amplifier in the range 50MHz – 300MHz and determine the resonance frequency, the maximum gain and the quality factor Q of the circuit.



Maximum gain 40,56 dB at 98,102 MHz, Bandwidth 2,1 MHz, Q=46,72

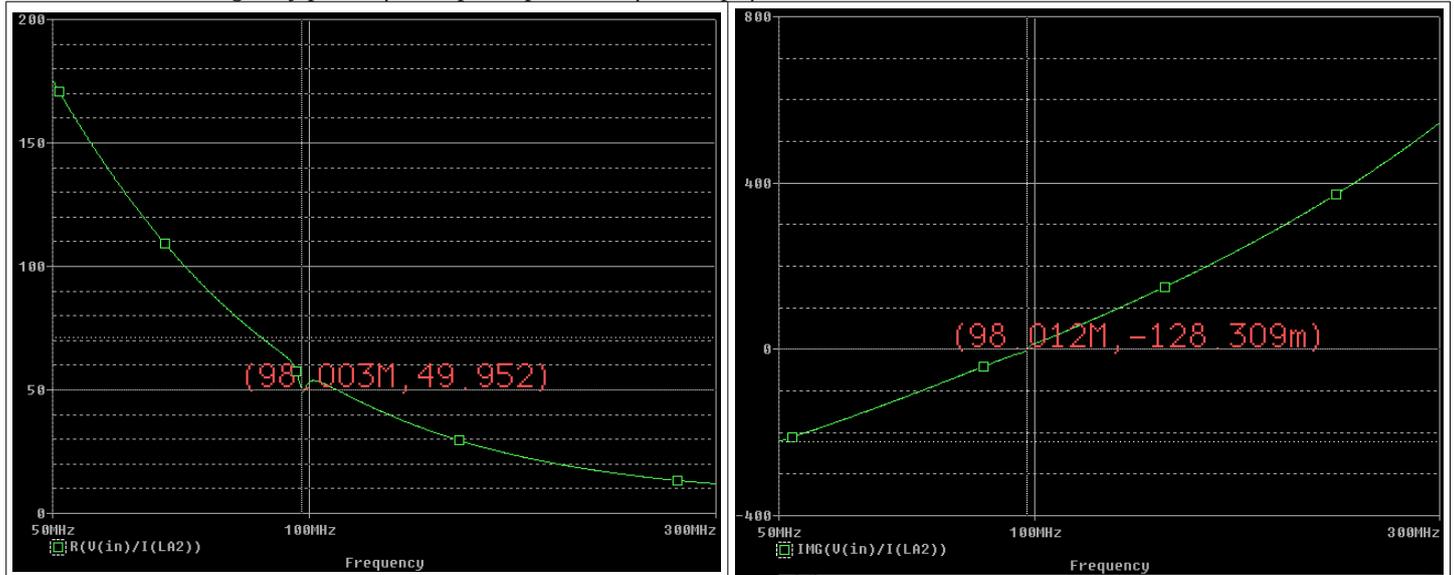Plot the real and imaginary parts of the input impedance of the amplifier.



Real part of input impedance with input MN = 49,95

Imaginary part of input impedance with input MN = -0,128

Comment on the results.

It is possible to note that using the output matching network based upon  $R_s=2000$ , it was necessary to change the input L matching network.

**03 – LOW NOISE AMPLIFIERS FOR FM RECEIVERS**

18/10/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)

04/06/2020 (rev.1 exam 12/06/2020)

**POINT 5, 6**

In order to increase the circuit selectivity, insert the input transformer TX2 with an input inductance of 100nH and an unitary transformation ratio together with the capacitor CT2.


Compute the values of the capacitance CT1 and capacitance CT2 in order to have the minimum and maximum resonance frequencies at 88MHz and 108MHz.

Resonant frequency = 88 MHz  
 CT1\_max=CT2\_max=33,3 pF


Resonant frequency = 108 MHz  
 CT1\_min=CT2\_min=20,1pF

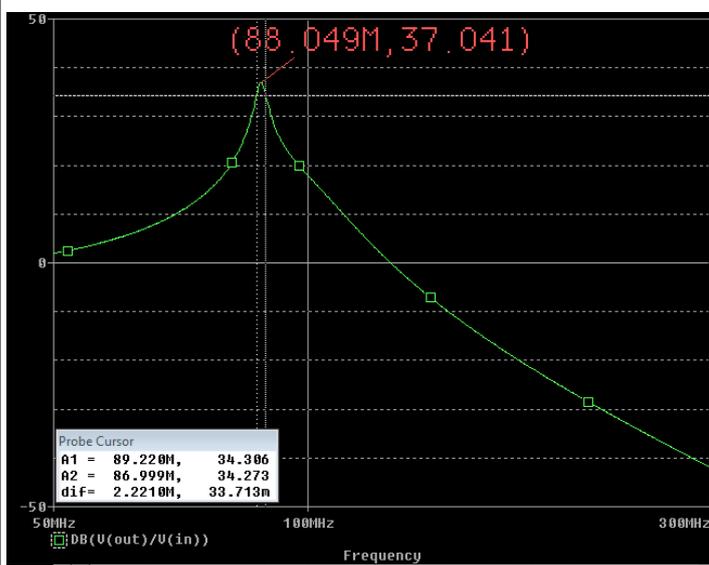**POINT 7**

Simulate the circuit obtained and determine the gain at 88MHz and 108MHz, respectively.



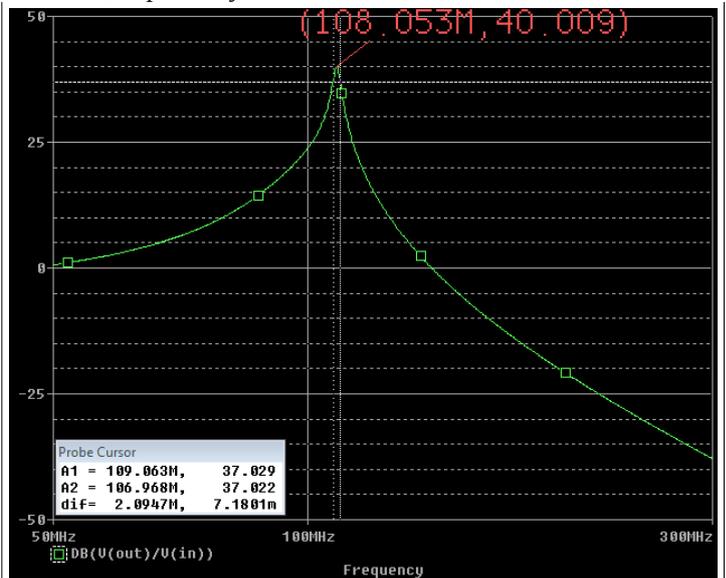Maximum gain 37,04 dB at 88,049MHz  
 Bandwidth 2,22 MHz  
 Q=39,66



Maximum gain 40 dB at 108,053 MHz  
 Bandwidth 2,09 MHz  
 Q=51,7

**03 – LOW NOISE AMPLIFIERS FOR FM RECEIVERS**


18/10/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)

04/06/2020 (rev.1 exam 12/06/2020)


**POINT 8**

Perform a transient analysis on the circuit designed. Impose a sinusoidal input generator with amplitude of 1mV and frequency 88MHz. Moreover, set the value of the capacitances in order to get the resonance at 88MHz. Display the input and output voltages. Measure the distortion of the amplifier.

frequency=88MHz, amplitude=1mV

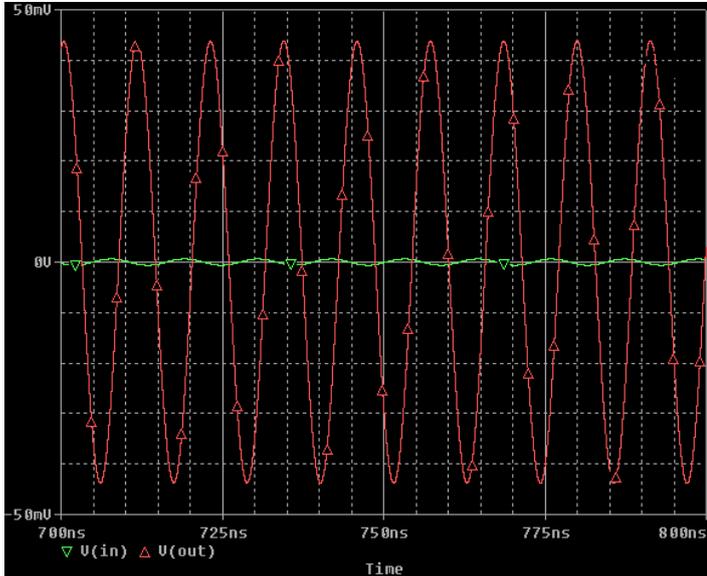

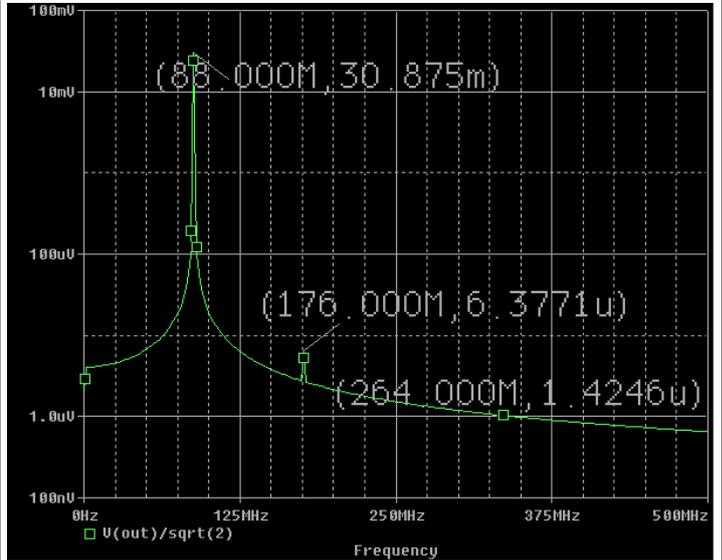
Vin\_peak=0,618 mV  
 Vout\_peak=43,9 mV  
 Linear gain = 71,03  
**db gain = 37,02**




Vrms at first harmonic =30,875mV  
 Vrms at second harmonic =6,377uV  
 Vrms at third harmonic =1,425uV  
**THD=0,021%**

Repeat the analysis with an input signal of 10mV.

frequency=88MHz, amplitude=10mV

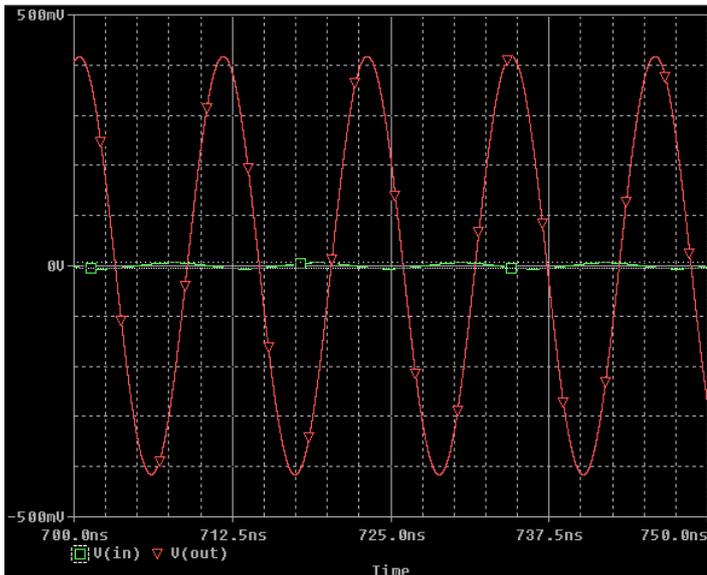

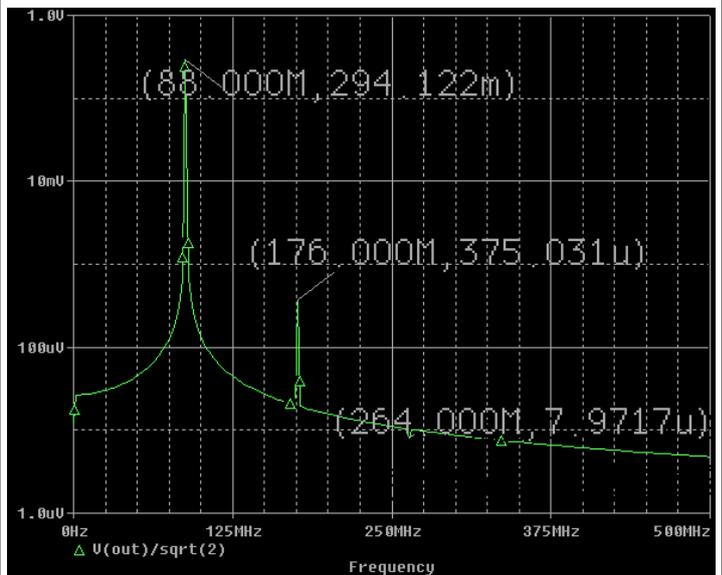Vin\_peak=6,24 mV  
 Vout\_peak=418,05 mV  
 Linear gain = 66,99  
**db gain = 36,52**



Vrms at first harmonic = 294,122mV  
 Vrms at second harmonic = 375,031uV  
 Vrms at third harmonic = 7,972uV  
**THD=0,127%**


**03 – LOW NOISE AMPLIFIERS FOR FM RECEIVERS**

18/10/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)


04/06/2020 (rev.1 exam 12/06/2020)

Repeat the analysis with an input signal of 100mV.

frequency=88MHz, amplitude=100mV

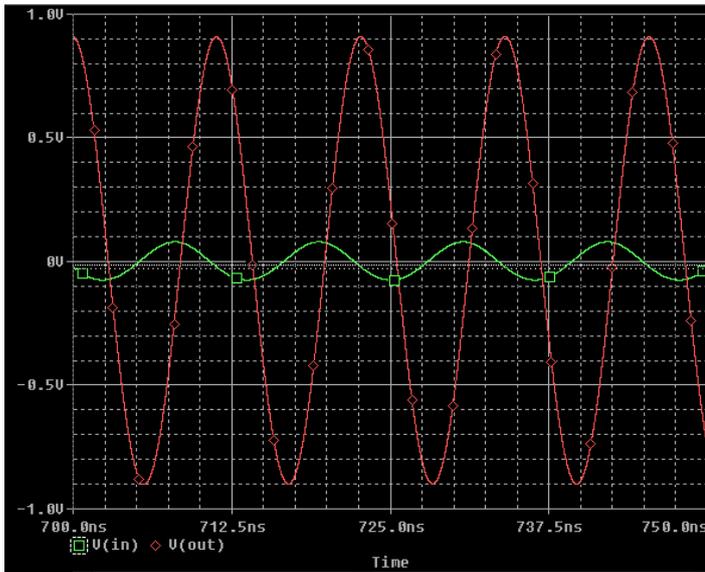

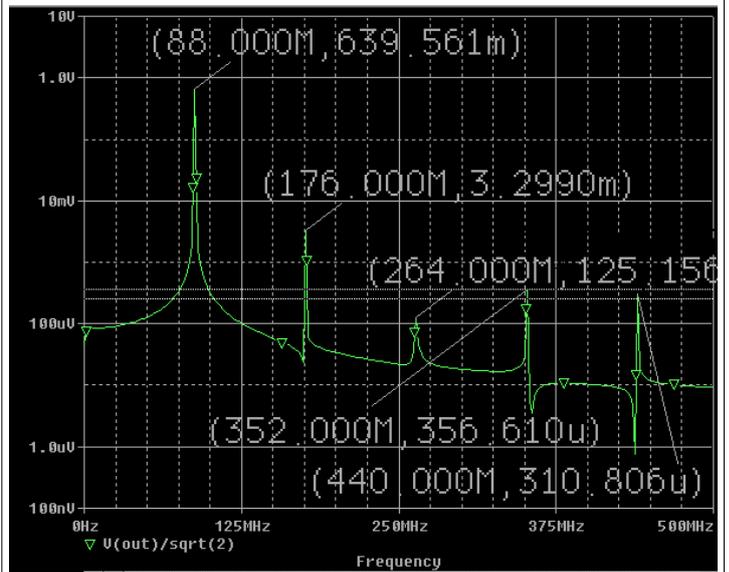
Vin\_peak=79,70 mV  
 Vout\_peak=910,80 mV  
 Linear gain = 11,43  
**db gain = 21,16**




Vrms at first harmonic = 693,561mV  
 Vrms at second harmonic = 3,299mV  
 Vrms at third harmonic = 125,156uV  
 Vrms at fourth harmonic = 356,61uV  
 Vrms at fifth harmonic = 310,806uV  
**THD=0,48%**

Impose a sinusoidal input generator with amplitude of 1mV and frequency 98MHz. Moreover, set the value of the capacitances in order to get the resonance at 98MHz. Display the input and output voltages. Measure the distortion of the amplifier.

frequency=98MHz, amplitude=1mV

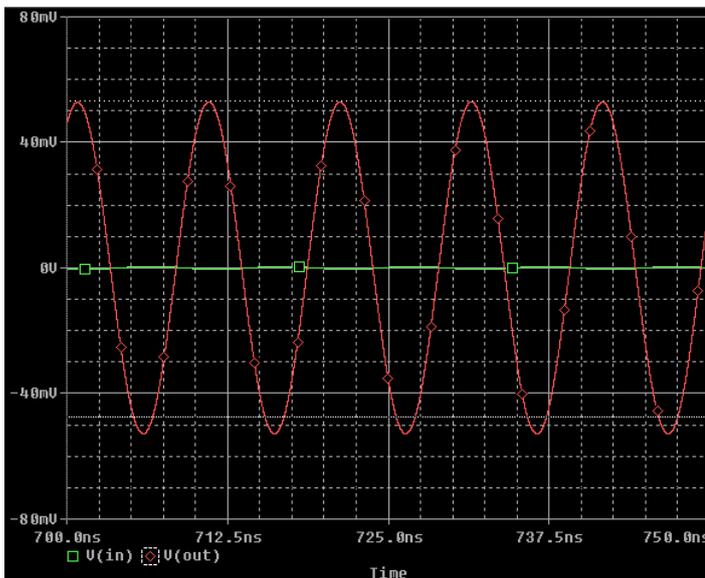

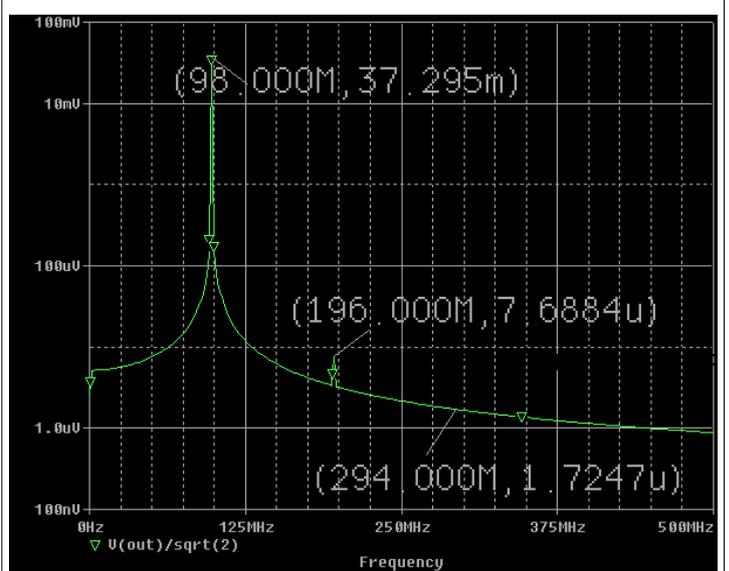Vin\_peak=0,499 mV  
 Vout\_peak=53,089 mV  
 Linear gain = 106,39  
**db gain = 40,54**



Vrms at first harmonic =37,295mV  
 Vrms at second harmonic =7,688uV  
 Vrms at third harmonic =1,725uV  
**THD=0,021%**


**03 – LOW NOISE AMPLIFIERS FOR FM RECEIVERS**

18/10/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)


04/06/2020 (rev.1 exam 12/06/2020)

Repeat the analysis with an input signal of 10mV.

frequency=98MHz, amplitude=10mV

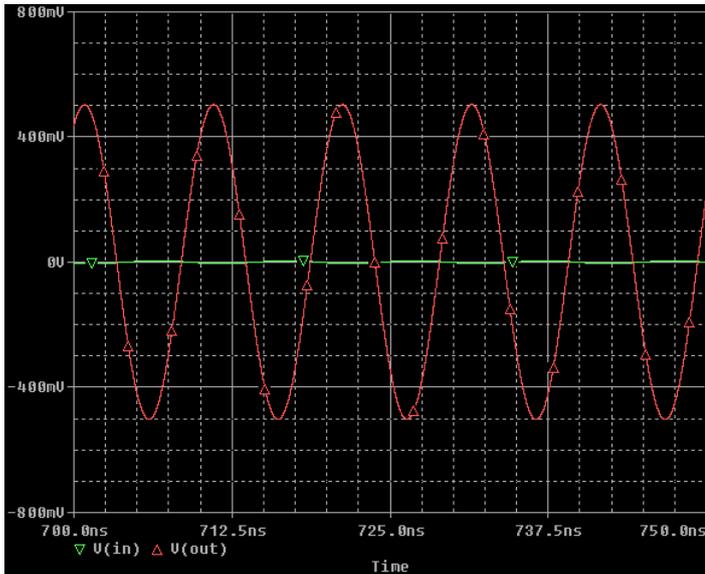

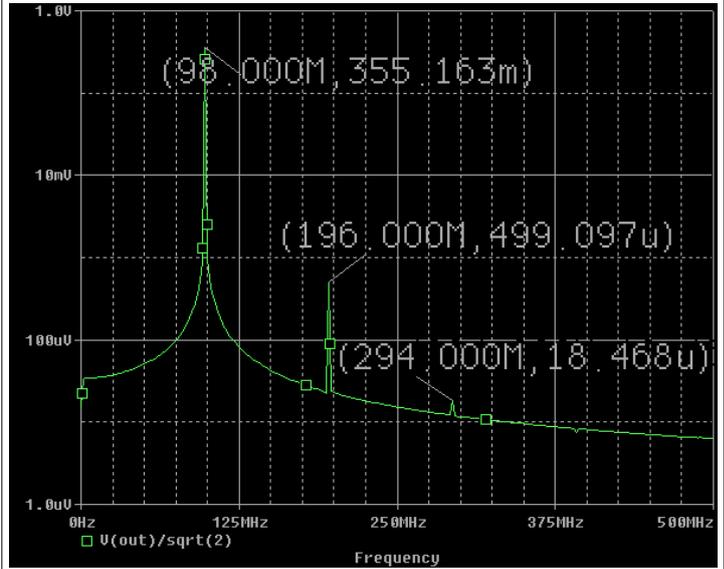
Vin\_peak=4,90 mV  
 Vout\_peak=504,934mV  
 Linear gain = 103,05  
**db gain = 40,26**




Vrms at first harmonic = 355,163mV  
 Vrms at second harmonic = 499,097uV  
 Vrms at third harmonic = 18,468uV  
**THD=0,14%**

Repeat the analysis with an input signal of 100mV.

frequency=98MHz, amplitude=100mV

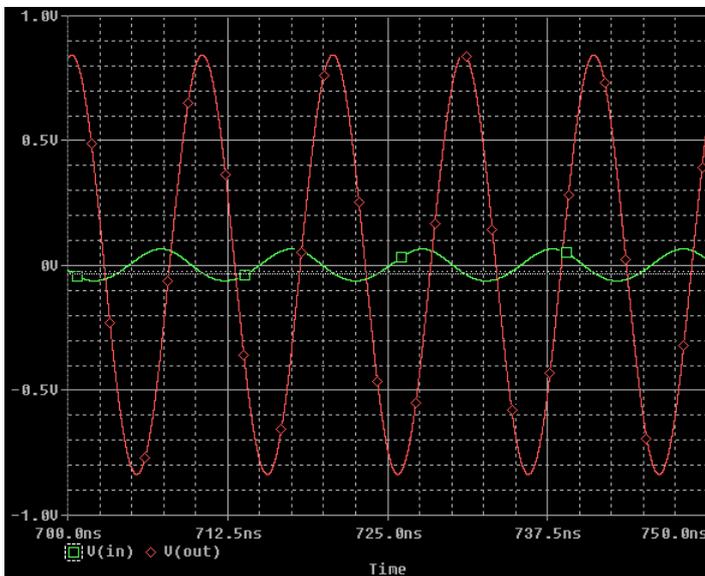

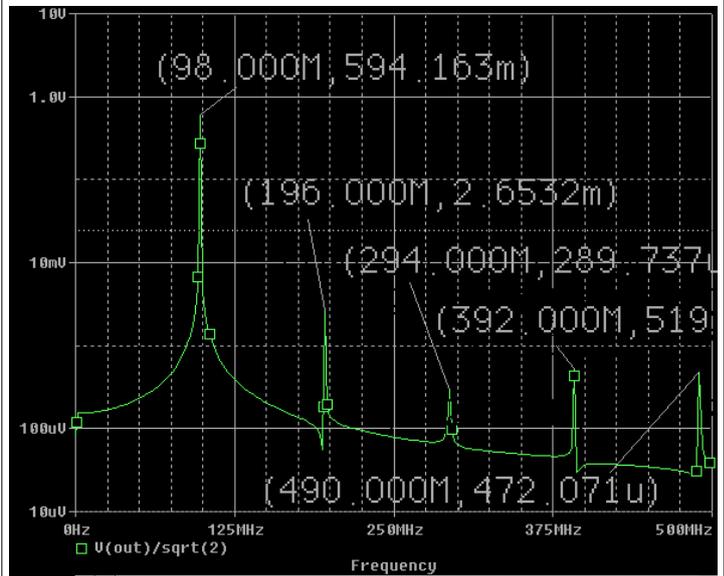Vin\_peak=66,486 mV  
 Vout\_peak=846,205 mV  
 Linear gain = 12,73  
**db gain = 22,09**



Vrms at first harmonic = 594,163mV  
 Vrms at second harmonic = 2,653mV  
 Vrms at third harmonic = 289,737uV  
 Vrms at fourth harmonic = 519,377uV  
 Vrms at fifth harmonic = 472,071uV  
**THD=0,46%**


**03 – LOW NOISE AMPLIFIERS FOR FM RECEIVERS**

18/10/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)


04/06/2020 (rev.1 exam 12/06/2020)

Impose a sinusoidal input generator with amplitude of 1mV and frequency 108MHz. Moreover, set the value of the capacitances in order to get the resonance at 108MHz. Display the input and output voltages. Measure the distortion of the amplifier.

frequency=108MHz, amplitude=1mV

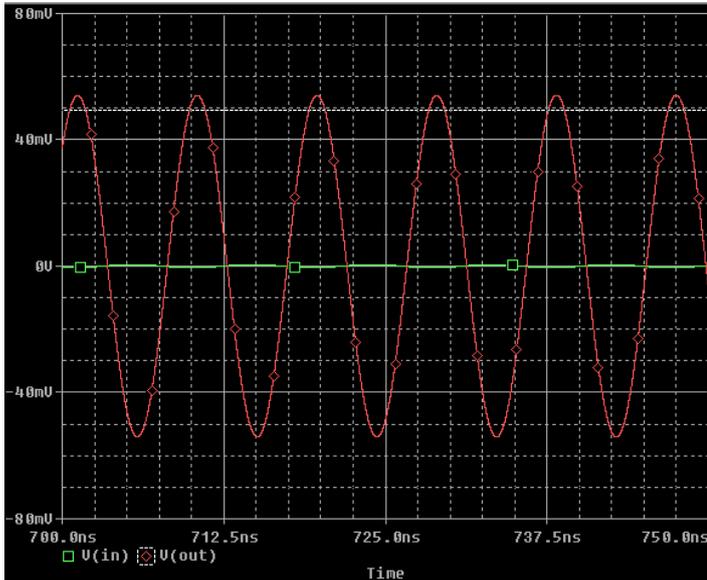


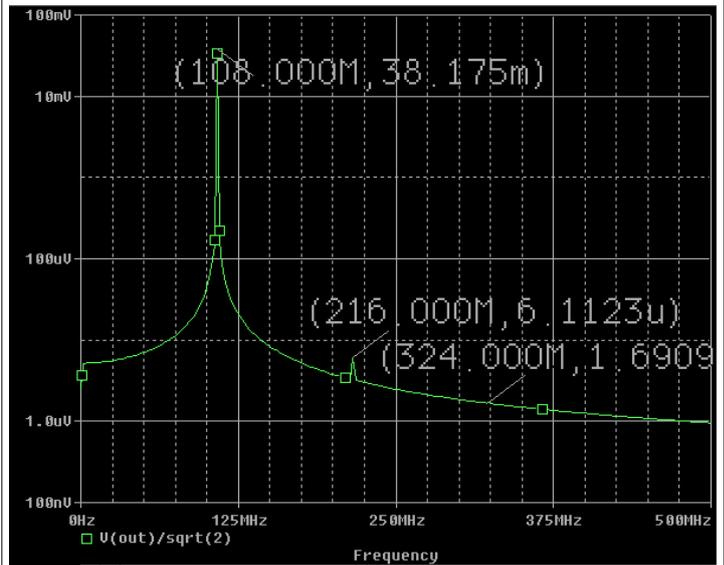Vin\_peak=0,542 mV  
 Vout\_peak=54,308 mV  
 Linear gain = 100,20  
**db gain = 40,02**




Vrms at first harmonic =38,175mV  
 Vrms at second harmonic =6,112uV  
 Vrms at third harmonic =1,691uV  
**THD=0,017%**

frequency=108MHz, amplitude=10mV

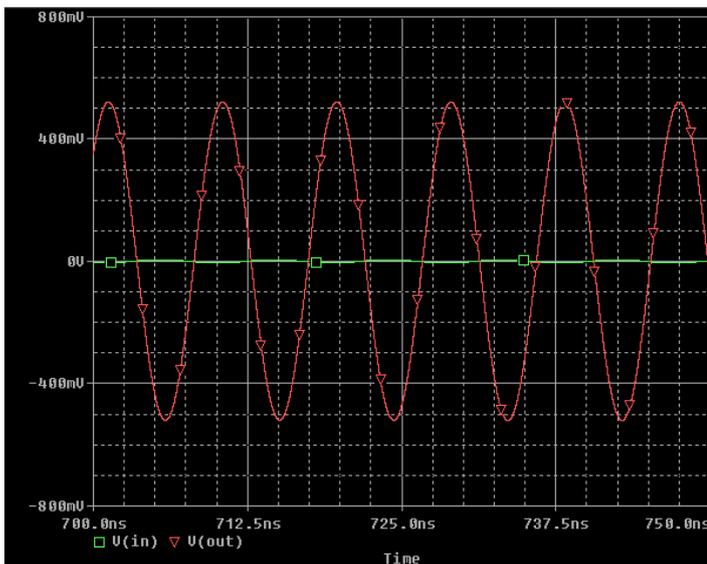

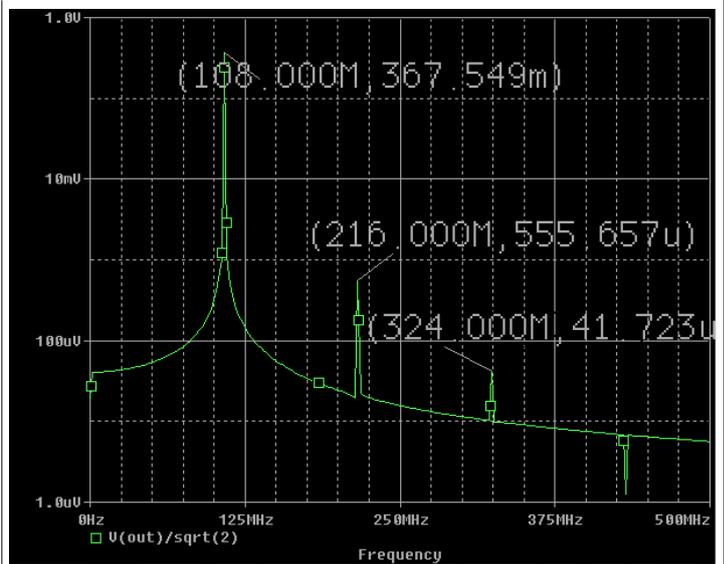Vin\_peak=5,296 mV  
 Vout\_peak=522,538 mV  
 Linear gain = 100,20  
**db gain = 40,02**




Vrms at first harmonic =367,549 mV  
 Vrms at second harmonic =555,657 uV  
 Vrms at third harmonic =41,723 uV  
**THD=0,15%**

**03 – LOW NOISE AMPLIFIERS FOR FM RECEIVERS**


18/10/2018 – Diego Tuzi – 50435 – [diego.tuzi@studentmail.unicas.it](mailto:diego.tuzi@studentmail.unicas.it)

04/06/2020 (rev.1 exam 12/06/2020)

frequency=108MHz, amplitude=100mV

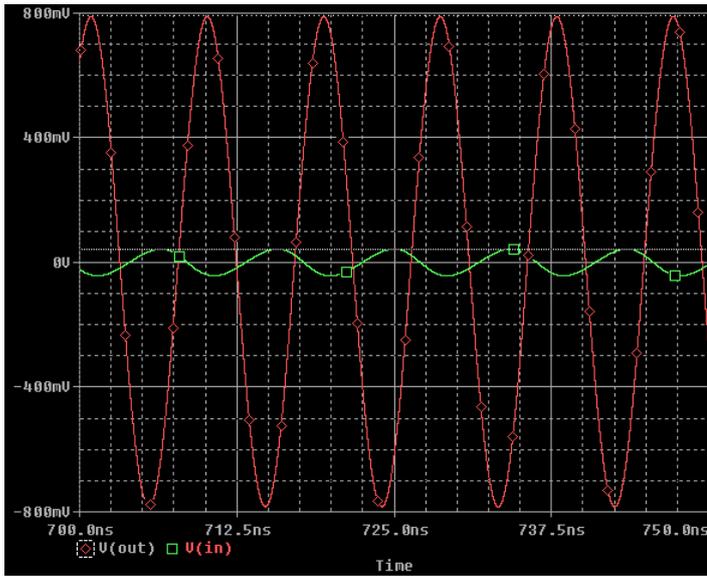

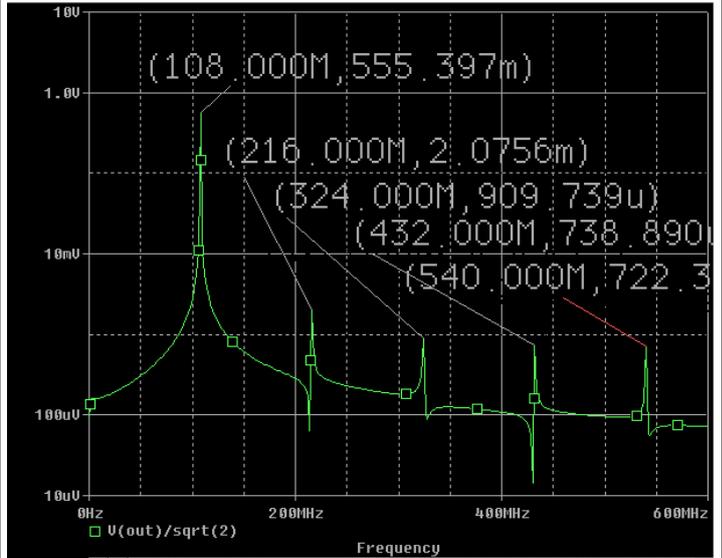Vin\_peak=43,793 mV  
 Vout\_peak=792,726 mV  
 Linear gain = 98,67  
**db gain = 25,15**



Vrms at first harmonic = 555,397 mV  
 Vrms at second harmonic = 2,076 mV  
 Vrms at third harmonic = 909,739 uV  
 Vrms at fourth harmonic = 738,890 uV  
 Vrms at fifth harmonic = 722,387 uV  
**THD=0,45%**

**POINT 9**

Extract CP 1dB , IIP3 and OIP3 from data obtained in the previous step for the frequency 88MHz.

